



CIS1910 Discrete Structures in Computing (I)
Winter 2019, Lab 4 Notes


*Here are recommended practice exercises. Many have been covered in Lab 4.
Note that the examples and exercises listed in blue come from the following textbook:
“Discrete Mathematics and Its Applications,” by Rosen, Mc Graw Hill, 7th Edition*

A. BOOLEAN ALGEBRA AND CIRCUIT DESIGN


Consider the Boolean algebra $(\{0,1\},+, \cdot, -)$, as seen in class (slide 2.11). The Boolean operations $+$, \cdot and $-$ can then be defined by the tables below. In this lab, the symbol $+$ will read “or” instead of “plus”, the symbol \cdot will read “and” instead of “dot”, and the symbol $-$ will read “not” instead of “bar”. Moreover, we will give \cdot a higher precedence than $+$.

| | | | | | | | |
|-----|-----|-------|-----|-----|-------------|-----|-----------|
| x | y | $x+y$ | x | y | $x \cdot y$ | x | \bar{x} |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 |
| 0 | 1 | 1 | 0 | 1 | 0 | 1 | 0 |
| 1 | 0 | 1 | 1 | 0 | 0 | | |
| 1 | 1 | 1 | 1 | 1 | 1 | | |


This Boolean algebra is at the basis of *circuit design*. A computer is made up of a number of circuits. The basic elements of circuits are *gates*. Typically, there are one or more inputs to a gate, and only one output. Gate inputs are driven by voltages having two nominal values (e.g., 0V and 5V); these values are represented by the symbols 0 and 1 respectively. The output of a gate also provides two nominal values of voltage only. Here are common gates:

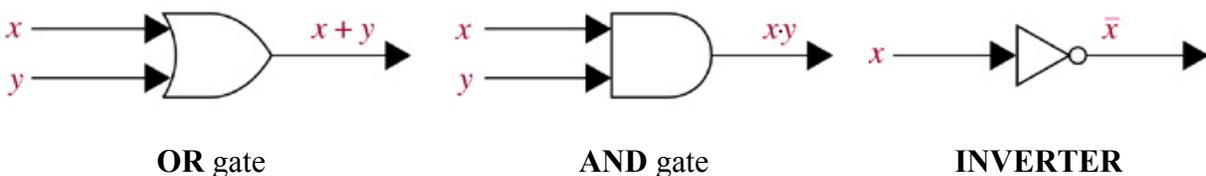

1. Consider the circuit below:

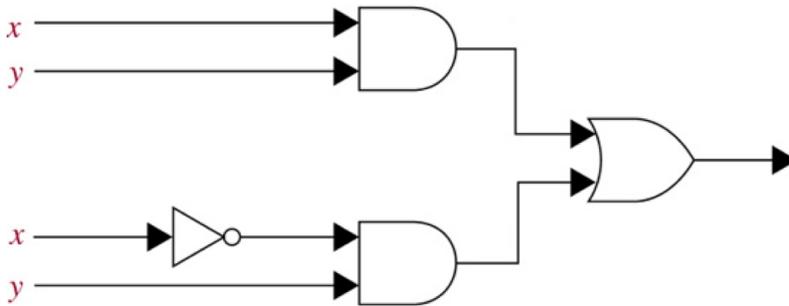

It can also be represented as follows:

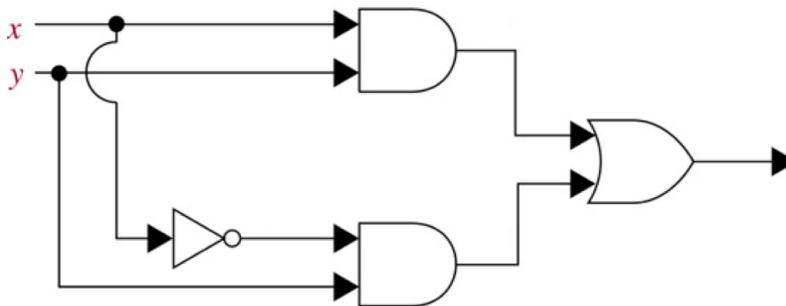

What is the output to this circuit?

2. Exercises 1, 3 and 5 from Section 12.3 of the textbook

3. (a) Example 1 p. 823

(b) Draw the tables that correspond to these circuits.

4. (a) Construct the circuit that produces the output $x \cdot y + x \cdot z + y \cdot z$.

(b) Draw the table that corresponds to this circuit.

(c) Example 2 p. 825

5. Example 3 p. 825

6. Consider the Boolean functions F and G defined by the table below.

| x | y | z | $F(x,y,z)$ | $G(x,y,z)$ |
|-----|-----|-----|------------|------------|
| 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 | 1 |
| 1 | 1 | 0 | 0 | 0 |
| 1 | 1 | 1 | 1 | 1 |

(a) Show that $F(x,y,z)$ can be expressed as a sum of minterms of degree 3. This sum is called the *sum-of-products expansion* of F.

(b) Construct the circuit that produces the output $F(x,y,z)$.

(c) Note that the sum-of-products expansion of F involves 6 operations: 1 sum, 4 products, 1 complementation. *Minimize* F, i.e., find an expression for $F(x,y,z)$ that involves a minimum number of operations.

(d) Construct the circuit that produces the output $x \cdot z$.

(e) Show that $G(x,y,z)$ can be expressed as a product of maxterms of degree 3 (this product is called the *product-of-sums expansion* of G), and minimize G.

7. (a) For any positive integer n and for any Boolean function F of degree n , it is possible to find an expression for $F(x_1, x_2, \dots, x_n)$ that involves no other Boolean operations than those in the set $\{+, \cdot, \bar{}\}$. Explain. We say that $\{+, \cdot, \bar{}\}$ is *functionally complete*.

(b) Let \downarrow be the Boolean operation defined by $x \downarrow y = \overline{x+y}$, for any elements x and y of B . This operation is called the *NOR* operation. Show that for any x and y of B we have: $\bar{x} = x \downarrow x$ and $x \cdot y = (x \downarrow x) \downarrow (y \downarrow y)$ and $x + y = (x \downarrow y) \downarrow (x \downarrow y)$.

(c) Is $\{\downarrow\}$ functionally complete?

(d) The Boolean expression $x \cdot \bar{y} + z$ involves three distinct Boolean operations: $+$, \cdot and $\bar{}$. Find an equivalent expression that involves \downarrow only.

B. PROPOSITIONAL LOGIC

A **propositional expression** is a finite sequence of symbols. The accepted symbols are T (which denotes a proposition that is true), F (which denotes a proposition that is false), p, q, r, etc. (which denote propositional variables), \neg , \wedge , \vee , \rightarrow , \leftrightarrow , etc. (which denote propositional operations) and brackets. The sequence should make sense, i.e., it should become a proposition once specific propositions are considered. For example, T, p, $\neg q$, $p \vee F$, $q \wedge \neg p$, $p \rightarrow [(\neg q) \vee r]$ are propositional expressions, while $\vee pq$, $p \wedge \vee q \neg$ and $)p \vee (q]$ are not. Note that a truth table can be attached to any propositional expression.

1. Section 1.1 of the textbook

(a) Examples 1, 2, 3, 4, 5, 6

(b) Because conditional statements play such an essential role in mathematical reasoning, a variety of terminology is used to express $p \rightarrow q$. For example:

| | | |
|----------------|--------------------|-------------------------------------|
| “if p, then q” | “q if p” | “p is sufficient for q” |
| “if p, q” | “q when p” | “a sufficient condition for q is p” |
| “p implies q” | “q unless not p” | “q is necessary for p” |
| “p only if q” | “q follows from p” | “a necessary condition for p is q” |

Examples 7 and 10

2. Section 1.2

(a) Examples 1 and 2

(b) Translating sentences in natural language (such as English) into propositional expressions is an essential part of hardware and software **system specification**. System and software engineers take requirements in natural language and produce precise and unambiguous specifications that can be used as the basis for system development.

Example 3